

**Minor Exam.**  
**B.Tech. (IT)-4th Sem.**  
**Subject: STLD**

**Time Duration:1 hour**

**Max. Marks:20**

**Each question carry equal marks.**

1. What is universal gate? Define NAND gate is a universal gate.
2. Design full adder using half adder.
3. Minimise the following logic function using K-map.  
 $f(A, B, C, D) = \sum m(1, 3, 7, 8, 10, 11, 12, 15) + d(0, 2, 5)$
4. Design 3 bit binary-to-gray code converter.